



## KENYATTA UNIVERSITY

UNIVERSITY EXAMINATIONS 2011/2012

SECOND SEMESTER EXAMINATION FOR THE DEGREE OF BACHELOR OF  
SCIENCE IN ELECTRICAL AND ELECTRONIC ENGINEERING

### EEE 204 CIRCUIT THEORY II

DATE: Thursday 12<sup>th</sup> April 2012

TIME: 8.00a.m – 10.00a.m

#### INSTRUCTIONS:

Answer **Question 1** and any other **Two** questions

Show all working in a neat and legible manner

#### Question 1 (Compulsory) – 30 marks

- a. Given the RC network in figure 1 below, determine
- An expression for the voltage transfer function of the network [5 marks]
  - Sketch the magnitude and phase response of the system. How would you characterize the network? [3 marks]
  - Given that  $R = 50 \text{ k}\Omega$  and  $L = 100 \text{ mH}$ , determine the cut-off frequency [2 marks]

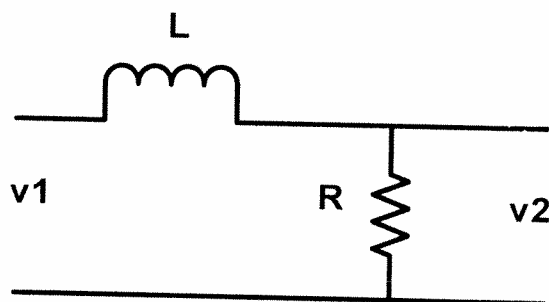


Figure 1

b. A sinusoidal voltage  $v(t) = 150 \cos(1000t + 10^\circ) V$  is connected across a passive circuit with an impedance  $Z = |Z| \angle \theta$  resulting in a current  $i(t) = 5 \cos(1000t - 50^\circ) A$ . Provide the complete power information i.e. Power factor,  $P_{av}$ , Q and S. [7 marks]

c. A periodic time varying current  $i(t)$  passes through a  $0.5 \mu F$  capacitor. Find and plot:

i. The instantaneous power  $p(t)$  entering the capacitor [6 marks]

ii. Energy  $w(t)$  stored in the capacitor [3 marks]

Where  $i(t)$  is described analytically for one period as

$$i(t) = \begin{cases} 1 \text{ mA} & ; 0 < t < 1 \text{ ms} \\ -1 \text{ mA} & ; 1 < t < 2 \text{ ms} \end{cases}$$

d. When one coil of a magnetically coupled pair has a current of 5 A, the resulting fluxes  $\phi_{11}$  and  $\phi_{12}$  are 0.2 mWb and 0.4 mWb respectively. If the turns are  $N_1 = 500$  and  $N_2 = 1500$ , find  $L_1$ ,  $L_2$ ,  $M$  and the coefficient of coupling  $k$ .

[4 marks]

## Question 2 - (20 marks)

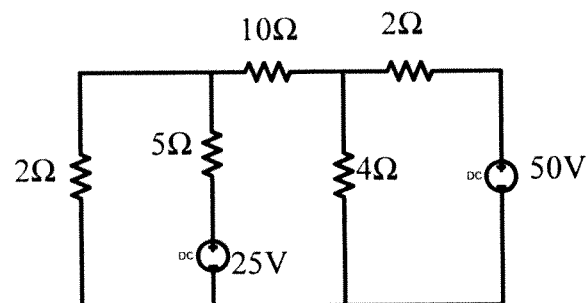


Figure 2

a. For the circuit shown in figure 2,

i. Write the mesh current matrix equation and solve for the three mesh currents

[7 marks]

ii. Repeat part (i) above using the node voltage method

[7 marks]

- b. For the circuit given in figure 1 ( $R = 50 \text{ k}\Omega$  ,  $L = 100 \text{ mH}$  ), and assuming zero initial conditions, determine the response of the circuit to a unit step input. Clearly indicate the transient and the steady state parts of the response. [6 marks]

**Question 3 - (20 marks)**

- a. Show that for a series resonant circuit, the resonant frequency is given by  $\omega_0 = \frac{1}{\sqrt{LC}}$  [5 marks]

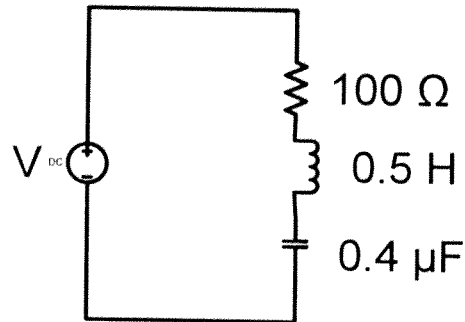


Figure 3

- b. For the RLC series circuit shown in figure 3, find
- The resonant frequency [1 mark]
  - Upper and lower half power frequencies  $\omega_h$  and  $\omega_l$  [6 marks]
  - Bandwidth of the circuit  $\beta$  [2 marks]
- c. Find the resonant frequency of the LC tank circuit of figure 4 if  $R = 2000\Omega$  ,  $C = 40\mu F$  ,  $L = 100 \text{ mH}$  [6 marks]

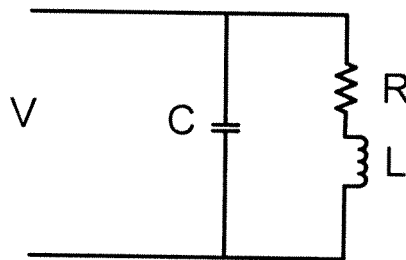


Figure 4

**Question 4 - (20 marks)**

- a. Find average power delivered to an impedance of  $Z = 50 + j12 \Omega$  from a sinusoidal voltage source with  $V_{eff} = 330 \text{ V}$  . Also find the power factor. [6 marks]

- b. Determine the total power information for three parallel connected loads specified as follows:
- > Load 1 – 250 VA,  $\text{pf} = 0.5$  lagging
  - > Load 2 – 180 W,  $\text{pf} = 0.8$  leading
  - > Load 3 – 300 VA, 100 Var (inductive)
- i. Calculate real power (P), reactive power (Q) and apparent power (S) for each load. Draw the power triangles of the three loads [7 marks]
- ii. Calculate total P, Q, S and PF for the total load. Draw the combined power triangle [7 marks]

**Question 5 - (20 marks)**

- a. What are the advantages of 3-phase power distribution? [6 marks]
- b. A 3-phase, ABC system with effective line voltage  $V = 240 \text{ V}$  has a  $\Delta$  connected load of  $Z_{AB} = 25\angle 90^\circ \Omega$ ,  $Z_{BC} = 15\angle 30^\circ \Omega$  and  $Z_{CA} = 20\angle 0^\circ \Omega$ . Obtain the line currents and the total power in the system. Draw the phasor diagram for the system [14 marks]