



KENYATTA UNIVERSITY

UNIVERSITY EXAMINATIONS 2011/2012

SECOND SEMESTER EXAMINATION FOR THE DEGREE OF BACHELOR OF
SCIENCE IN ELECTRICAL AND ELECTRONICS ENGINEERING

EEE 307: NETWORK ANALYSIS AND SYNTHESIS

DATE: FRIDAY, 13TH APRIL 2012

TIME: 8.00 A.M. – 10.00 A.M.

INSTRUCTIONS

- (i) This paper contains **FIVE (5)** questions.
- (ii) Answer all question in Section **A** and any **TWO** questions from each Sections **B**.

SECTION A

1a) Define the following terms as used in graph theory

- i. Branch
- ii. Node
- iii. Tieset
- iv. Cutset
- v. Incidence matrix
- vi. **b) i)** Draw the oriented graph of networks shown in **figure 1**

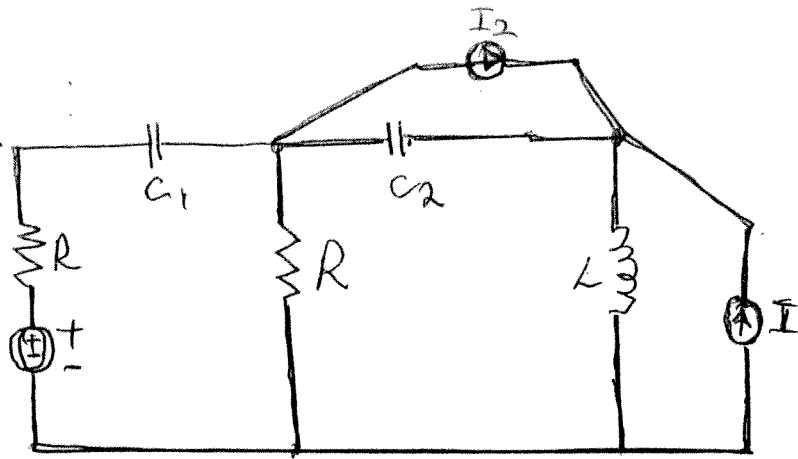


Figure 1.

- ii) Draw all possible trees and co-trees of oriented graph above (bi) (4mks)
 c) i) For the network shown in **figure 2**, determine the Z parameter (4mks)

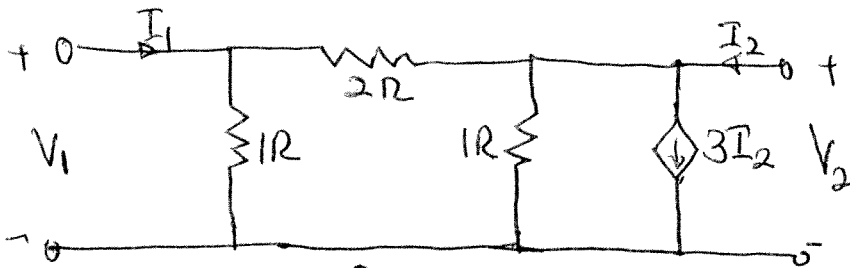


figure 2

- ii) What is the necessity for an isolating transformer when two-port networks are connected in series or parallel (2mks).

d) i) Define Hurwitz Polynomial (2mks)

ii) An impedance function is given by

$$Z = \frac{(s+1)(s+4)}{5(s+2)(s+5)}$$

Find the RC representation of Foster -I (4mks)

e) Design a constant high pass filter (both π and T networks) having a cut-off frequency of 2KHZ with load resistance of 200Ω (6mks)

SECTION B

2a) Write the loop matrix equation for the network shown in **figure 3** above. Selected three to be represent by branch with C1 and L (15mks)

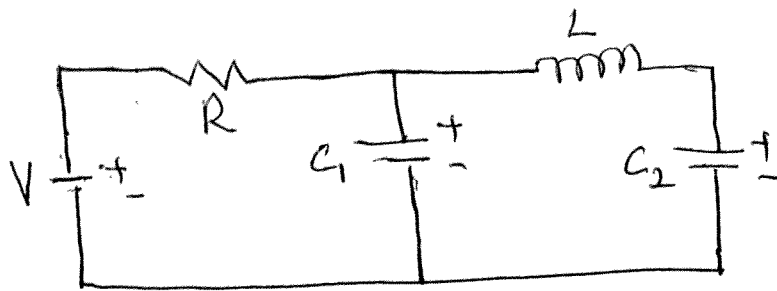


figure 3.

b)i) Explain the concept of duality (2mks)

ii) Draw the Dual of the network shown below in the **figure 4** (3mks)

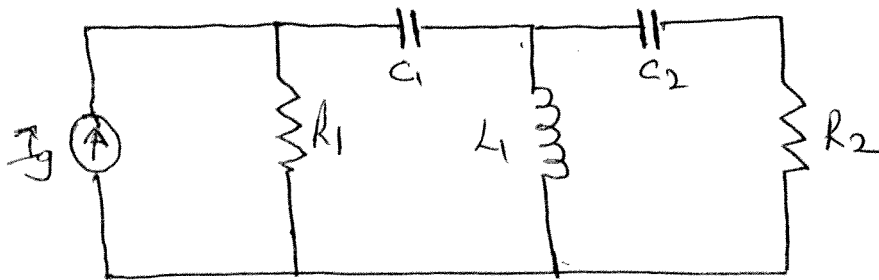


figure 4.

3a) For the circuit network shown in **figures 5**, obtain the Y parameters (8mks)

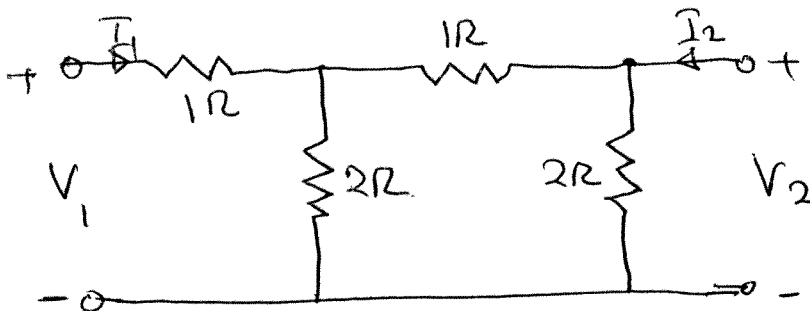


figure 5.

ii) The Y -parameters of two-port network are

$$Z_{11} = 0.5S, Z_{22} = 0.2S, Z_{12} = Z_{21} = 0.25S$$

Computes transmission parameter (6mks)

b)i) For the network shown in **figure 6**, calculate the h -parameters. (6mks)

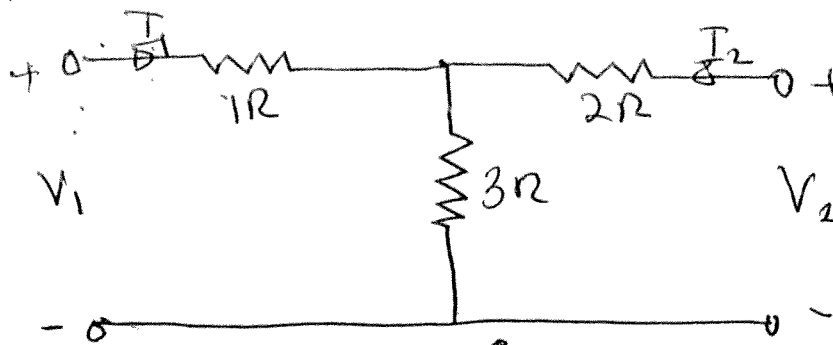


figure 6.

4a) An admittance function is give as

$$Y(s) = \frac{4s^2 + 6s}{s + 1}$$

Realize the network using Cauer's first and second form (10mks)

b) i) An impedance function has the pole-zero pattern as shown in **figure 7**. If $Z(-2) = 3$, synthesize the impedance in Foster second form (6mks).

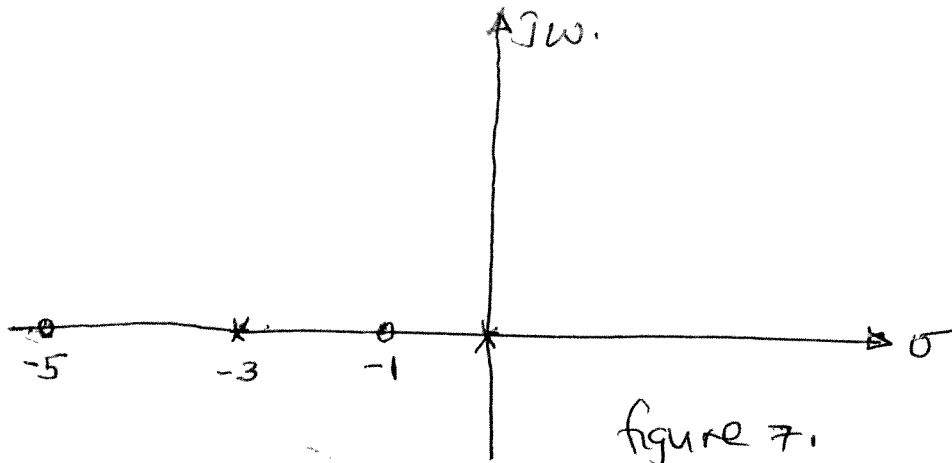


figure 7.

ii) Find the range of values of a so that

$$P(s) = s^4 + s^3 + 9s^2 + 2s + 3$$
 is Hurwitz

5a) i) State any four advantages of active filters over passive filter (2mks)

ii) Design m-derived T and π networks low pass filter with nominal characteristic impedance $R_0 = 900\Omega$, cut off frequency $f_c = 0.9$ KHZ and infinite attenuation (or resultant) frequency $f_\infty = 1$ KHZ (8mks)

bi) State and prove the Maximum Power Transfer Theorem of an AC circuit (10mks).