



KENYATTA UNIVERSITY
UNIVERSITY EXAMINATIONS 2010/2011
FIRST SEMESTER EXAMINATION FOR THE DEGREE OF BACHELOR OF SCIENCE
IN COMPUTER ENGINEERING
SCE 213: CIRCUIT THEORY I

DATE: Tuesday 23rd November, 2010

TIME: 11.00 a.m. – 1.00 p.m.

INSTRUCTIONS


Attempt Questions ONE and any other TWO questions.

QUESTION ONE

(a) (i) Explain Kirchhoff's laws.

(2 Marks)

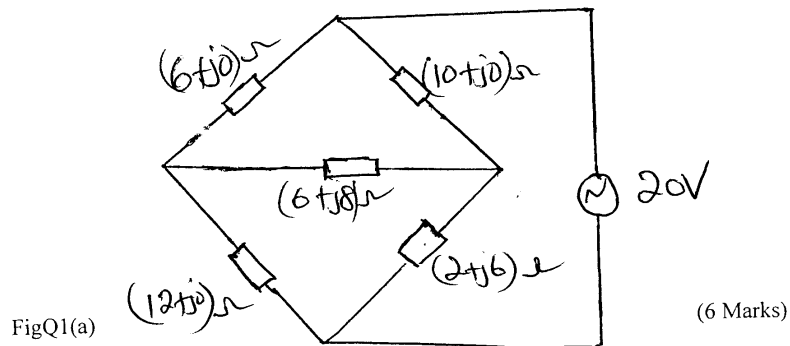(ii) For the network shown in Fig Q1(a) calculate the current in the $(6 + j8)$ impedance.



- (b) (i) Explain the Maximum Power Transfer Theorem. (3 Marks)
(ii) Describe why impedance matching is of importance in communication circuits. (3 Marks)

(c) (i) Explain what is meant by the following terms:

(I) frequency


(II) peak factor

(III) R.M.S value

(IV) amplitude

(4 Marks)

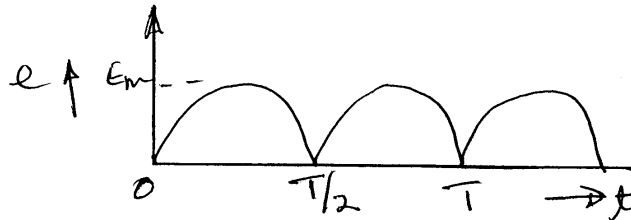(ii) Determine the average and r.m.s values of the full wave rectified sine wave voltage shown in Fig Q1(c)(ii). (4 Marks)



FigQ1(c)(ii)

(d) (i) Explain what is meant by the power factor in an A.C circuit. (2 Marks)

(ii) A circuit having a resistance of 12Ω , an inductance of 0.15 H and a capacitance of $100 \mu\text{F}$ in series is connected across a $100\text{V}, 50 \text{ Hz}$ supply. Calculate the impedance, current and phase difference between the current and the supply voltage. (3 Marks)

(e) Prove that the node voltage equations can be arranged into a general matrix form;

$$[Y][V] = [I]$$

Where $[Y]$ = symmetrix admittance matrix

$[V]$ = voltage source matrix.

(3 Marks)

QUESTION TWO

- a) Show that in all A.C circuit with a capacitor C the voltage lags the current by an angle of $\pi/2$.
- b) A coil of resistance 50Ω and inductance $0.318H$ is connected in parallel with a circuit computing a 75Ω resistor in series with a $159\mu f$ capacitor. The resulting circuit is connected to a $240V$, $50Hz$ A.C supply. Calculate the;
- Supply current
 - Circuit impedance resistance and reactance. (14 Marks)

QUESTION THREE

- a) The instantaneous values of two attending voltages are represented by $\ell_1 = 60\sin\theta$ volts and $\ell_2 = 40\sin(\theta - \pi/3)$ volts. Derive an expression for the instantaneous value of the
- Sum
 - Difference of these two voltages. (8 Marks)
- b) i) Determine the load impedance that can be connected across terminals A and B for maximum power transfer to the load impedance for the circuit shown in Fig 2(b). (8 Marks)
- Calculate the maximum power transferred to the load. (4 Marks)

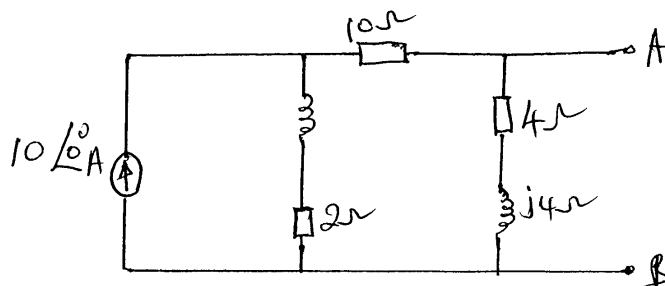


Fig 2(b)

QUESTION FOUR

- a) i) with the aid of circuit diagram explain Millinan's Theorem (4 Marks)
- ii) For the circuit shown in Fig Q 4(a) derive the mesh equation in matrix form. (6 Marks)

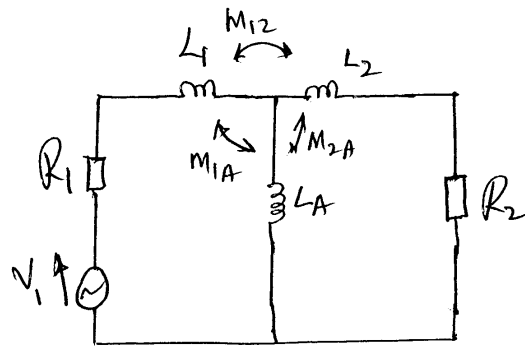


Fig Q 4(a)

- b) A network is arranged as shown in Fig Q 4(b). Calculate the value of the current in the 8Ω resistor. (10 Marks)

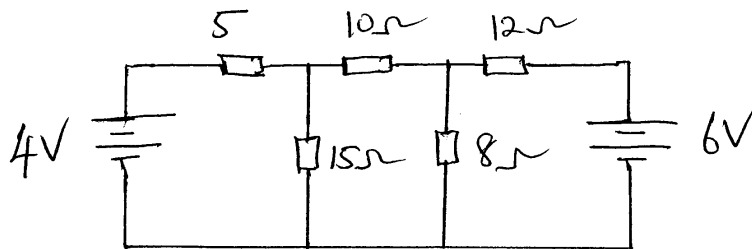


Fig Q 4(b)

QUESTION FIVE

- a) Briefly explain the impedance function as applied in steady state analysis in electric circuits
(4 Marks)
- b) For circuit shown in fig Q 5, determine;
- $z(j\omega)$
 - Given $\mu = \cos \omega t$, for $\omega = 9.9$, calculate the current in all the elements and I_s .
 - The value of ω_0 , for which I_s and v are in phase
 - ω_2 at which $|z(j\omega_2)| = |z(j\omega_1)|$
- (16 Marks)

