



KENYATTA UNIVERSITY

UNIVERSITY EXAMINATIONS 2011/2012

SECOND SEMESTER EXAMINATION FOR THE DEGREE OF BACHELOR
OF SCIENCE IN COMPUTER ENGINEERING

SCE 316: DIGITAL ELECTRONICS II

DATE: Friday, 13th April, 2012

TIME: 11.00 a.m. – 1.00 p.m.

-
- (i) This paper contains **FIVE** questions.
(ii) Answer question **1** and any other **TWO** questions
-

Question 1 (COMPULSORY)

a)

i) Explain the difference between an encoder and a decoder

(2 marks)

ii) How does a priority encoder differ from an ordinary encoder?

(1 mark)

b) What is a multiplexer?

(2 marks)

c) State THREE applications of multiplexers

(3 marks)

d) Draw a block diagram symbol and the truth table for a 1-line-8-line demultiplexer

(4 marks)

e) Give definitions of the following terms referred in DAC?

i) Accuracy

(2 marks)

ii) Settling time

(2 marks)

iii) Resolution

(2 marks)

f) A Certain clocked R-S Flip Flop has set up and hold times specified typically as $t_s = 30 \text{ ns}$ and $t_h = 5 \text{ ns}$

i) What is the minimum amount of time that the R and S inputs have to be HIGH before the CLK input transition occurs? **(1 mark)**

ii) How long must the R and S inputs remain in the HIGH state once the CLK transition occurs **(1 mark)**

Question 2:

a) Design a logic circuit for the **e** and **g** output of a BCD to 7 segment decoder with active LOW outputs showing the truth table and a simplified expression for each output **(10 marks)**

b) What is the advantage of an flash EPROM over a EEPROM? **(5 marks)**

c) Draw a block diagram of a 74150 data selector being used to solve the logic problem described by the Boolean expression $A'B'C'D + A'BCD + ABCD' + AB'C'D' + ABCD = Y$. **(5 marks)**

Question 3:

a) An analog voltage of the range of $-V$ to $+V$ is required to be converted into 3-bit 2's complement digital format. The digital value for 0 V should be 000 and the maximum quantization error should not exceed $\pm \text{LSB}$. Determine the quantization interval **(5 marks)**

b) Design a D/A converter for 4-bit digital inputs in 1's complement format **(5 marks)**

c) Explain the fundamental difference between A/D and D/A converters. **(3 marks)**

d) When the output of a flip-flop goes LOW, HIGH, LOW, HIGH on repeated clock pulses, it is in what mode of operation? **(2marks)**

Question 4:

Suppose an input to a recognizer circuit is given as **11100110100100110**. The recognizer circuit has only one input **X**. There is also one output **Z** which is a **1** when the desired pattern is realized/found. Using sequence recognizer to detect the pattern **1001**.

- What will be the output if one bit of input is supplied on every clock cycle
(5 marks)
- Design a JK flip flop based circuit with the state diagram shown in the Figure 4.1, show all your working including the final circuit diagram
(15 marks)

 


Figure4.1

Question 5:

Design a BCD to decimal decoder with the use of an active HIGH decoder. In your design show,

a) The truth table (5 marks)

b) Simplified expression for the outputs D0, D1 and D3 (5 marks)

c) What will be the expression for D0,D1, and D3 if you use an active LOW decoder? (5 marks)

d) There are two types of seven segment decoder displays i.e the Common Cathode and Common Anodes. Distinguish between the two? (5 marks)