



KENYATTA UNIVERSITY

UNIVERSITY EXAMINATIONS 2010/2011

**FIRST SEMESTER EXAMINATION FOR THE DEGREE OF BACHELOR OF
SCIENCE (COMPUTER SCIENCE)**

SCT 103: ELECTRONIC DEVICES AND CIRCUITS (NEW)

DATE: Monday, 22nd November, 2010

TIME: 8.00 a.m. – 10.00 a.m.

INSTRUCTIONS:

Answer question **ONE** and any other **TWO** questions.

QUESTION ONE

- a) Explain what a P-N junction is and how it is formed, clearly illustrating the biasing (3 marks)
- b) Discuss a brief theory of the following:
 - i) P-N junction diode (3 marks)
 - ii) Bipolar junction transistor (3 marks)
 - iii) Field effect transistor (3 marks)
 - iv) Operational amplifier (3 marks)
 - v) Comparison on Analog to digital and Digital to analog converters (4 marks)
 - vi) Using a well labeled circuit diagram, discuss the functionalities of a Wien bridge oscillator. (6 marks)
- c) List and explain the characteristics of the two mainly used semiconductor doping material (4 marks)
- d) Differentiate between oscilloscopes and multi-meters (1 mark)

QUESTION TWO

- a) Using a well-labeled diagram, discuss the biasing of a PNP and NPN transistor
(6 marks)
- b) Draw an output characteristic of a transistor, and use a load line to illustrate how a transistor is used as an amplifier
(6 marks)
- c) Differentiate between the following types of Field Effect Transistors:
 - i) MOSFET (2 marks)
 - ii) MESFET (2 marks)
 - iii) IGBET (2 marks)
 - iv) JFET (2 marks)

QUESTION THREE

- a) Use a circuit diagram, and an expression to show how an operational amplifier achieves the following function:
 - i) Adding (4 marks)
 - ii) Subtracting (4 marks)
 - iii) Comparator (4 marks)
- b) With an aid of a circuit diagram and a flow chart, explain how a Successive Approximation Analog to Digital Converter (ADC) functions. (8 marks)

QUESTION FOUR

- a) When using a oscilloscope, it was realized that the displayed signal amplitude is of low magnitude, and the signal was not stable. What two variables would be used to solve this problem
(6 marks)
- b) You are training a technician to use a multi-meter. Which three precautions would you advice the technician to observe while using the multi-meter?
(3 marks)
- c) List and explain any **FIVE** characteristics of an ideal operational amplifier
(5 marks)
- d) Using well labeled diagrams, differentiate between a high pass filter and a low pass filter
(6 marks)

QUESTION FIVE

- a) With an aid of a bias arrangement for N-channel JFET, explain the biasing and the operation of a JFET (6 marks)
- b) Draw the JFET output characteristics, clearly showing the ohmic, saturation, cut-off and break-down regions. (6 marks)
- c) With an aid of a circuit diagram, and a mathematical expression, explain how an operational amplifier is used as:
 - i) Differential amplifier (4 marks)
 - ii) Integrator (4 marks)